

Fig. 2: Suitable arrangement of phototransistor

 


Fig. 3: Pin configuration of transistor BC557

and connected in the circuit shown in Fig. 1. Fig. 2 shows the suitable arrangement of phototransistor.

The detected signal is amplified by transistor 2N2222 (T5) and further amplified by operational amplifier CA3140 (IC3). The reference voltage point for the operational amplifier is obtained by resistor divider network comprising R2 and R3. The output from pin 6 of IC3 is fed to pin 12 of microcontroller AT89C2051. Note that pins 12 and 13 of microcontroller AT89C2051 are the inputs (+ and -) of its internal analogue comparator. Pin 13 is adjusted to nearly half the supply voltage using a potential divider comprising resistor R7 and preset VR1 across the supply.

The pulses picked up by the phototransistor are sensed by the internal comparator of AT89C2051 and, through software, each pulse representing one rotation of the object is detected. By counting the number of such pulses, on an average per minute basis, the RPM is evaluated. It is displayed by a software routine to light up the LED segments of the 4-digit, 7-segment display.

## Circuit description

Fig. 1 shows the circuit of the microcontroller-based tachometer. The tachometer comprises AT89C2051 microcontroller, ULN2003 high-current Darlington transistor array, CA3140 operational amplifier, common-anode 7-segment (4-digit multiplexed) display and its four anode-driving transistors.

The AT89C2051 is a 20-pin, 8-bit microcontroller of Intel's 8051 family made by Atmel Corporation. Port-1 pins P1.7 through P1.2, and port-3 pin P3.7 are connected to input pins 1 through 7 of ULN2003. Port-1 pins are pulled up with 10-kilo-ohm resistor network RNW1. They drive all the seven segments of the display with the help of internal inverters.

Port-3 pins P3.0 through P3.3 of the microcontroller are connected to the base of transistors T1 through T4, respectively, to select one digit out of the four at a time and to supply anode-drive currents to the common anode pin of respective digit. Pin configuration of transistor BC557 is shown in Fig. 3.

When pin P3.0 of microcontroller IC1 goes low, it drives transistor T1 into saturation, which provides the

drive current to anode pin 6 of 4-digit, 7-segment, common-anode display DIS1. Similarly, transistors T2 through T4, respectively, provide supply to common-anode pins 8, 9 and 12 of DIS1. Thus microcontroller IC1 drives the segment in multiplexed manner using its port pins. This is time-division multiplexing process.

Segment data and display-enable pulse for display are refreshed every 5 ms. Thus, the display appears to be continuous even though it lights up one by one.

Switch S1 is used to manually reset the microcontroller, while the power-on-reset signal for the microcontroller is given by C1 and R6. A 12MHz crystal is connected to pins 4 and 5 of IC1 to

 


Fig. 4: A single-side, actual-size PCB layout for microcontroller-based tachometer

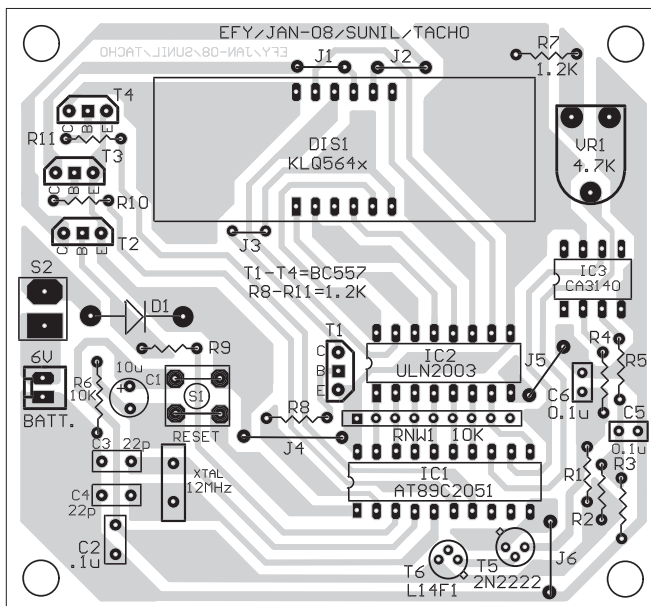


Fig. 5: Component layout for the PCB

generate the basic clock frequency for the microcontroller. The circuit uses a 6V battery for power supply or alternatively a mains derived low voltage supply. An actual-size, single-side PCB layout for the tachometer (Fig. 1) is shown in Fig. 4 and its component layout in Fig. 5.

## Testing

The source code of this article is available at <http://www.electronicsforu.com/efycodes/efy-codes.zip> at code file 'tacho.hex.' Using a programmer, load the code into the new chip AT89C2051. (Refer the May 2005 issue of EFY for article on programmer for 89C51 and 2051.) Then, fit it into the circuit board and after powering up the circuit, test it.

For testing, point the probe using

torchlight for illumination of the rotating object. For fans, use the light from behind. Hold the probe firmly so as to provide a steady, bright illumination on the object. Even an LED pen torch could be used here. Avoid the fluctuating background light from sources such as tubelight.

## Software

The software is written in Assembly language and assembled using 8051 cross-assembler. It is well commented and easy to understand. It uses AT89C2051's internal timer for measuring the period of one cycle of the rotation in units of 100 microseconds. Thus if the speed is 1500 rpm, it is 25 rps, and the time taken for one cycle is 40 ms.

The timer uses an interrupt to count

overflows every 100 microseconds and so the number counted by the timer program in this case will be '400.' This is divided by '600,000' (so many 100/ $\mu$ s present in a minute), giving a result of '1500.' This gives the rpm. These digits are displayed on the 4-digit, 7-segment display. To perform the division, subroutine UDIV32 is employed, which is a standard subroutine available for 8051 family for 32-bit number by 16-bit number division. It has an accuracy of 5 rpm in a 6000rpm count.

**EFY note.** The source code of this article is available at <http://www.electronicsforu.com/efycodes/efy-codes.zip> and will also be included in EFY-CD of February 2008 issue. ●

*Prof. K. Padmanabhan retired from Alagappa College of Technology, Guindy, Chennai*

## TACHO.ASM

```
$mod51
ORG 0H
AJMP 30H
ORG 0BH ;TIMER 0 INTERRUPT VECTOR
AJMP TIMER0ISR ;Timer 0 Interrupt service routine address
ORG 30H
MOV SP,#60H ;set stack pointer
MOV P3,#0FFH ;set all port 3 bits high to enable inputs also
MOV P1,#03 ;set port 1 to all zeros except bits 0,1
MOV TMOD,#01100001B ;TIMER 1 - MODE 2 COUNTER,TIMR-0 TO 16 bit timer
BEG: MOV TH0,#0ffh ;TIMER REG.0 IS SET TO 0, GIVES 64ms
MOV TL0,#99 ; timer low reg. is also so
setb et0
setb ea
mov 44h,#0
mov 45h,#0
acall delay
ajmp lowsig
delay: mov r2,#10
djnz r2,$ ;wait 20 us
ret
lowsig: jb p3.6,lowsig
call delay
jnb p3.6,$
setb tr0 ; start timer
mov c,p3.6 ;high begins
mov p3.5,c
acall delay
jb p3.6,$
mov c,p3.6 ;low now
mov p3.5,c
acall delay
jnb p3.6,$
mov c,p3.6 ;high begins again
mov p3.5,c
clr tr0 ;stop timer
clr et0 ;and interrupt by timer
mov r3,#0 ;number 600000 or 927c0 hex as Dividend
mov r2,#09h ; 9
mov r1,#27h ;27
mov r0,#0c0h ; c0
mov r5,#45h ;divisor is time for one cycle
mov r4,#44h
call UDIV32 ;divide 60000/t
mov 40h,r0
mov 41h,r1
mov r1,#41h
```

```
mov r2,#40h
CALL HEX2BCD
mov 50h,#0FFH
call refresh
disp: call refresh1
djnz 50h,disp ; so many times for a visible time limit
jmp beg
;16 Bit Hex to BCD Conversion for 8051 Microcontroller
;This routine is for 16 bit Hex to BCD conversion;
;Accepts a 16 bit binary number in R1,R2 and returns 5 digit BCD in ;R7,R6,R5,R4,R3(upto 64K )
Hex2BCD: ;r1=high byte, r7 most significant digit, R2 = LSByte
MOV R3,#00D
MOV R4,#00D
MOV R5,#00D
MOV R6,#00D
MOV R7,#00D
MOV B,#10D
MOV A,R2
DIV AB
MOV R3,B ;
MOV B,#10 ; R7,R6,R5,R4,R3
DIV AB
MOV R4,B
MOV R5,A
CJNE R1,#0H,HIGH_BYTE ; CHECK FOR HIGH BYTE
SJMPE ENDD
HIGH_BYTE: MOV A,#6
ADD A,R3
MOV B,#10
DIV AB
MOV R3,B
ADD A,#5
ADD A,R4
MOV B,#10
DIV AB
MOV R4,B
ADD A,#2
ADD A,R5
MOV B,#10
DIV AB
MOV R4,B
ADD A,#2
ADD A,R5
MOV B,#10
DIV AB
MOV R5,B
CJNE R6,#00D,ADD_IT
SJMPE CONTINUE
ADD_IT: ADD A,R6
CONTINUE: MOV R6,A
DJNZ R1,HIGH_BYTE
MOV B,#10D
MOV A,R6
```

```
DIV AB
MOV R6,B
MOV R7,A
ENDD: ret
DISP1:
REFRESH: ; content of 18 to 1B memory locations are output on LEDs
; only numbers 0 to 9 and A to F are valid data in these locations
MOV 18H,r3 ; least significant digit
MOV 19H,r4 ; next significant digit
MOV 1AH,r5
MOV 1BH,R6 ; most significant digit (max:9999)
RET
refresh1:
MOV R0,#1bh ; 1b,1a,19,18, holds values for 4 digits
MOV R4,#8 ; pin p3.3_0 made low one by one starts with 18
mov r7,#2 ; decimal pt.on 3rd digit from left (2 nd fromright)
PQ2: CALL SEGDISP
dec R0
mov a,r4
rrc a
mov r4,a
jnc pQ2
PV3:RET
SEGDISP:mov dptr,#ledcode
MOV A,@R0
ANL A,#0FH
MOVC A,@A+dptr
segcode:MOV R5,A
ORL A,#03H ; WE WANT TO USE PORT 1 BITS 0 AND 1 FOR INPUT ANLOG
; so retain them high
S3: MOV P1,A ; SEGMENT_PORT
MOV A,R5 ;we use p3.7 for the segment 'a' of display
RRC A ;so get that bit D0into carry
rrc a
mov p3.7,c ;segment 'a';
S1: MOV A,R4 ; get digit code from r4 00001000
cpl a ;11110111
rrc a ;11110111-1
mov p3.0,c ; output to drive transistors for digit lighting
rrc a ;11110111-1
mov p3.1,c
rrc a ;11110111-1
mov p3.2,c
rrc a ;11110111-1 yes low makes left most digit show msdigit
```

```

mov p3.3,c
S5:
S4: ACALL DELAY1 ; let it burn for some time
MOV A,#0ffh ; extinguish the digit after that time
MOV P3,A ; to prevent shadow
s6: RET
ledcode:DB 7EH,0CH,0B6H,9EH,0CCH,0DAH,0FAH
;these are code for the numbers 0 to 9 and A to F
DB 0EH,0FEH,0CEH,0EEH,0F8H,72H,0BCH,0F6H,
0E2H
DELAY1:MOV 55h,#0ffh ; 1ms
N: NOP
DJNZ 55h,N
RET
TIMER0ISR:mov th0,#0ffh
mov tl0,#-90 ; in 100 us steps
push acc
mov a,#1
clr c
add a, 44h ;count time btwn pulses
mov 44h,a
mov a,#0
addc a,45h ;add carry to most sign. byte
mov 45h,a
pop acc
reti
; subroutine UDIV32
;32 bit /16 bit to 32 bit quotient and remainder un-
signed
;input r3,r2,r1,r0 = dividend X
;input r5,r4 = divisor y
;output r3-r0 = quotient Q of X/Y
;r7,r6,r5,r4 =remainder
alters acc, flags
UDIV32: push 08 ;save reg. bank 1
push 09
push 0AH
push 0BH
push 0CH
push 0DH
push 0EH
push 0Fh
push dpl
push dph

```

```

push B
setb RS0 ;select reg.bank 1
mov r7,#0
mov r6,#0
mov r5,#0
mov r4,#0
mov B,#32 ;set loop count
div_lp32:clr RS0 ;select reg.bank 0
clr C
mov a,r0 ;shift highestbit of X
rlc a
mov r0,a
mov a,r1 ;shift next bit of X
rlc a
mov r1,a
mov a,r2 ;shift next bit of X
rlc a
mov r2,a
mov a,r3 ;shift next bit of X
rlc a
mov r3,a
setb rs0 ;reg. bank 1
mov a,r4 ;lowest bit of remainder
rlc a
mov r4,a
mov a,r5 ;shift next bit of rem
rlc a
mov r5,a
mov a,r6 ;shift next bit of rem
rlc a
mov r6,a
mov a,r7 ;shift next bit of rem
rlc a
mov r7,a
mov a,r4
clr C
subb a,04
mov dpl,a
mov a,r5
subb a,5
mov dph,a
mov a, r6
subb a,#0
mov 06,a

```

```

mov a,r7
subb a,#0
mov 07,a
cpl C
jnc div_321
mov r7,7
mov r6,6
mov r5,dph
mov r4,dpl
div_321: mov a,r0
rlc a
mov r0,a ; shift result bit into partial quotient
mov a,r1
rlc a
mov r1,a
mov a,r2
rlc a
mov r2,a
mov a,r3
rlc a
mov r3,a
djnz B,div_lp32
mov 7,r7
mov 6,r6
mov 5,r5
mov 4,r4
mov 3,r3
mov 2,r2
mov 1,r1
mov 0,r0
clr rs0
pop B
pop dph
pop dpl
pop 0Fh
pop 0EH
pop 0Dh
pop 0Ch
pop 0bh
pop 0ah
pop 09
pop 08
ret
END

```



## Let Us Get Ahead Together

### Tell Me More About Advertising Opportunities in EFY Magazine

I am aware that EFY Magazine presents umpteen advertising opportunities. I too would like to explore the various options available for my organisation, so that I can help it grow in terms of sales and brand presence. My details are mentioned below:

Name \_\_\_\_\_ Organisation \_\_\_\_\_ Designation \_\_\_\_\_  
 Address \_\_\_\_\_ City \_\_\_\_\_ Pincode \_\_\_\_\_  
 Phone \_\_\_\_\_ Fax \_\_\_\_\_ E-mail \_\_\_\_\_

I would like to have a one-to-one meeting

- I would like to have a one-to-one meeting with someone from the EFY team.
- Please send me your marketing kit containing all necessary details.



**Please mail/fax this form to:**  
**EFY Enterprises Pvt Ltd**  
 D-87/1, Okhla Industrial Area, Phase-I, New Delhi 110020  
 Tel: 011-26810601/2/3; Fax: 011-26817563  
 Email: efymkt@efyindia.com; Website: www.efyindia.com